

B.Sc. (semester -3)

Subject : Physics

Course : USO3CPHY22

BASIC SOLID STATE ELECTRONICS

UNIT 3: FEEDBACK IN AMPLIFIERS

Lecture 2

Prof.Sandip V. Dholakia
Physics Department
Bhavan's College, Dakor



- ❖ Quick Revision of Lecture 1
- ❖ How negative feedback is Advantageous
- ❖ Voltage gain of Series Voltage Negative feedback Amplifier
- ❖ Stabilization Of GAIN

- ❖ **Quick Revision of Lecture 1**
- ❖ Feedback is the process of taking part of output signal and feeding it back to the input circuit
- ❖ two types of feedback (1) Negative feedback (2) Positive feedback
- ❖ When the feedback signal is out of phase with the input signal and thus opposes it, it is called negative feedback
- ❖ When the feedback signal is in phase with the input signal and thus aids it, it is called positive feedback.
- ❖ Amplifier negative feedback types
 - If the feedback network samples the output voltage, it is *voltage feedback*.
 - If it samples the output current, it is *current feedback*.
 - The feedback signal can be connected in series or in parallel with the signal source and the amplifier input terminals,
 - so called **SERIES FEEDBACK** and **SHUNT or PARALLEL FEEDBACK**.


❖ Quick Revision of Lecture 1

- there are FOUR types of negative feedback in amplifier circuits:
 - Series voltage feedback
 - Series current feedback
 - Shunt or Parallel voltage feedback
 - Shunt or Parallel current feedback
- In voltage feedback, the input terminals of the feedback network are in parallel with the load, and the output voltage appears at the input terminals of the feedback block.
- Whereas in current feedback, the input terminals of the feedback network are in series with the load, and the load current flows through the input of the feedback block.
- A Series feedback tends to increase the input impedance of the amplifier..
- Shunt or Parallel feedback tends to decrease the input impedance of the amplifier..
- A Voltage feedback tends to decrease the output impedance of the amplifier...
- Current feedback tends to decrease the output impedance of the amplifier...
- Most of the amplifier demands higher input impedance and lower output impedance
- which are both met in Series Voltage Feedback Amplifier...so...they widely used....

❖ **HOW NEGATIVE FEEDBACK IS ADVANTAGEOUS?**

- The negative feedback in amplifiers reduces the gain.
- However, it improves the performance of amplifier in several ways as shown below:-
 - (i) It improves the stability of amplifier gain
 - (ii) It reduces the distortion and noise.
 - (iii) It increases the input impedance.
 - (iv) It decreases the output impedance
 - (v) It increases the bandwidth.

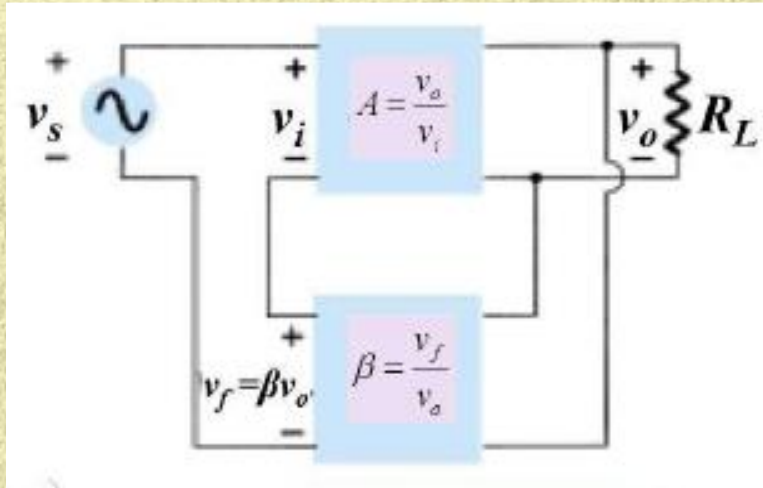❖ Voltage gain of Series Voltage Negative feedback Amplifier



- Here, a portion of output voltage feedback in series to the input.
- Negative feedback results overall gain reduction.
- If there is no feedback ($V_f = 0$). The voltage gain of the amplifier is:-

$$A = \frac{v_o}{v_s} = \frac{v_o}{v_i}$$

If V_f is connected in series with the input, then

$$V_i = V_s - V_f \text{ Since } V_o = AV_i = A(V_s - V_f) = AV_s - AV_f \dots = AV_s - A(\beta V_o) \\ \Rightarrow V_o (1 + \beta A) = AV_s \dots \therefore \frac{V_o}{V_s} = \frac{A}{1 + \beta A}$$

So overall voltage gain with feedback is $A_f = \frac{v_o}{v_s} = \frac{A}{1 + \beta A}$

➤ In case of Positive feedback then above equation assumes in below form

$$A_f = \frac{A}{1 - A\beta}$$

➤ From above equation we can say that in case of Negative feedback the Voltage gain of amplifier Decreases ... However it is desirable for Good performance.....

➤ From above equation we can say that in case of Positive feedback the Voltage gain of amplifier Increases ... This type of feedback is used in Oscillator circuits.....

❖ STABILIZATION OF GAIN

➤ The gain of negative feedback amplifier is given by equation $A_f = \frac{A}{1+A\beta}$..(1)

➤ Here if we make $A\beta \gg 1$ then $A_f = \frac{A}{A\beta} = \frac{1}{\beta}$...(2)

➤ then A_f becomes independent of internal gain A.

➤ to estimate small change in the gain of amplifier we differentiate equ (1) with respect to A... so we get

$$\rightarrow \frac{dA_f}{dA} = \frac{1}{(1+A\beta)^2}$$


$$\text{➤ } \therefore dA_f = \frac{dA}{(1+A\beta)^2} \dots (3)$$

➤ Dividing equ (3) by equ (1), we get

$$\text{➤ } \frac{dA_f}{A_f} = \frac{dA}{(1+A\beta)^2} \times \frac{1+A\beta}{A} \quad \therefore \frac{dA_f}{A_f} = \frac{1}{1+A\beta} \times \frac{dA}{A} \dots\dots (4)$$

➤ Here since $(1+A\beta) \gg 1$, the percentage change in A_f is very much less than the percentage change in A...

❖ Reduction in Distortion and Noise

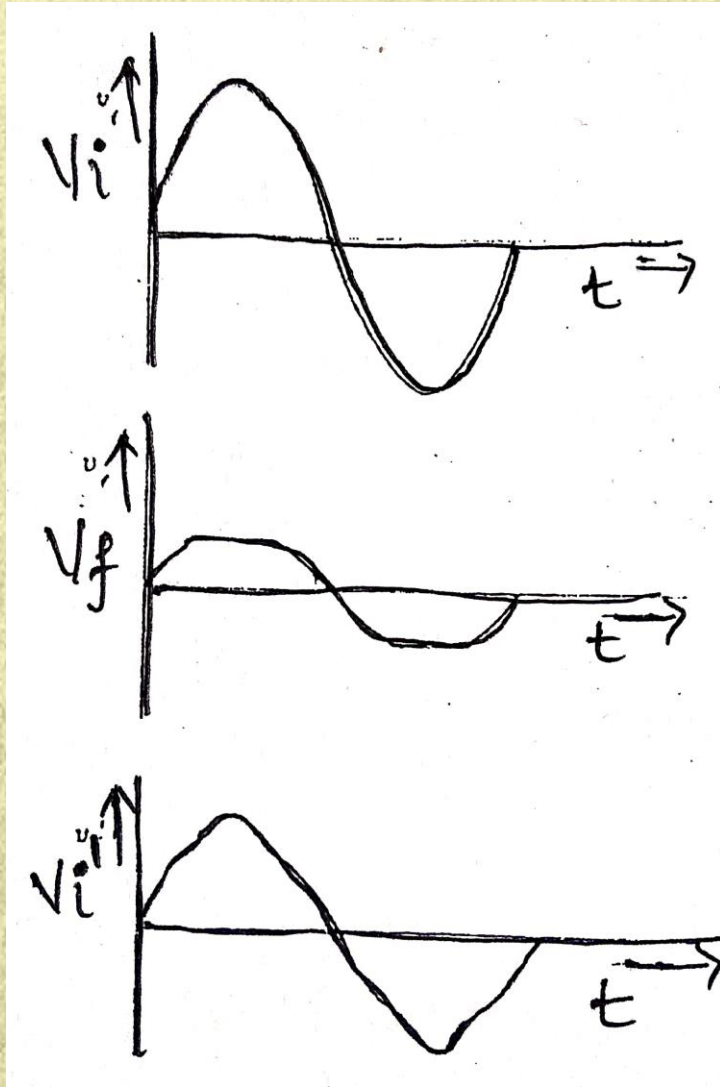

- The figure shows the voltage waveforms corresponding to the input voltage V_i , the feedback voltage V_f and the net input voltage to the amplifier v_i' in case of a negative feedback amplifier..
- The voltage V_f gets subtracted from the input voltage V_i to make the net input V_i' to the amplifier,
- Actually when input voltage v_i is amplified by the amplifier, its peak is flattened and it remains flattened even after it passes through the feedback network and becomes V_f .
- This V_f is then subtracted from V_i and gives the resulting output V_i' with more higher peak
Thus every time input is predistorted to compensate for the flattening caused by the amplifier.

- 
- IN NEXT LECTURE WE TALK MORE ABOUT REMAINING ADVANTAGE OF NEGATIVE FEEDBACK AMPLIFIER
 - PLEASE TRY TO LEARN FROM BOTH LECTURES
 - AND MAKE NOTES



THANK YOU.....